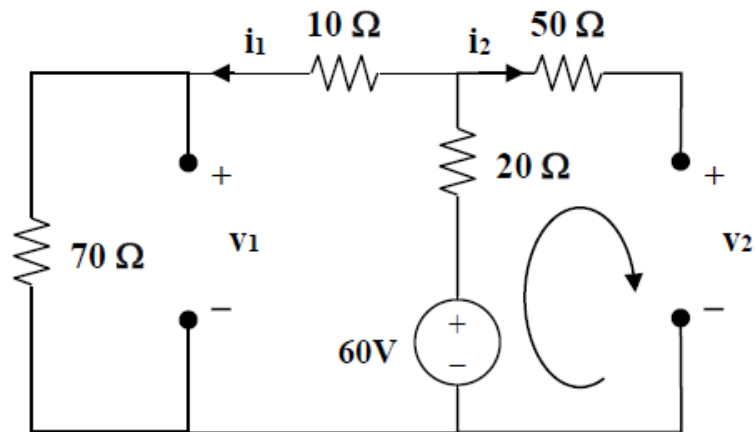


Solution 6.13

Under dc conditions, the circuit becomes that shown below:



$$i_2 = 0, i_1 = 60/(70+10+20) = 0.6 \text{ A}$$

$$v_1 = 70i_1 = 42 \text{ V}, v_2 = 60 - 20i_1 = 48 \text{ V}$$

Thus, $v_1 = 42 \text{ V}$, $v_2 = 48 \text{ V}$.

Solution 6.32

In the circuit in Fig. 6.64, let $i_s = 4.5e^{-2t}$ mA and the voltage across each capacitor is equal to zero at $t = 0$. Determine v_1 and v_2 and the energy stored in each capacitor for all $t > 0$.

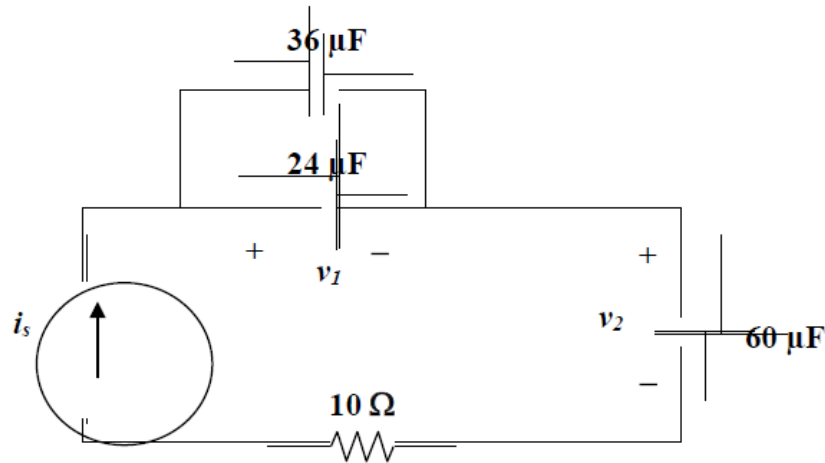


Figure 6.64
For Prob. 6.32.

Solution

Combining the $36\ \mu\text{F}$ with the $24\ \mu\text{F}$ we get $60\ \mu\text{F}$ which leads to $v_1 = \frac{1}{60\mu} \int_0^t 4.5e^{-2\tau} m d\tau$
 $= [37.5 - 37.5e^{-2t}] \text{ V} = v_2$.

$$(v_1)^2 = [(37.5)^2 - 2(37.5)^2e^{-2t} + (37.5)^2e^{-4t}] = 1406.25[1 - 2e^{-2t} + e^{-4t}] = (v_2)^2$$


$$w_{24} = 0.5 \times 24 \times 10^{-6} (v_1)^2 = \mathbf{16.875[1 - 2e^{-2t} + e^{-4t}] \text{ mJ}}$$

$$w_{36} = 0.5 \times 36 \times 10^{-6} (v_1)^2 = \mathbf{25.31[1 - 2e^{-2t} + e^{-4t}] \text{ mJ}}$$

$$w_{60} = 0.5 \times 60 \times 10^{-6} (v_2)^2 = \mathbf{42.19[1 - 2e^{-2t} + e^{-4t}] \text{ mJ}}$$

Solution 6.46

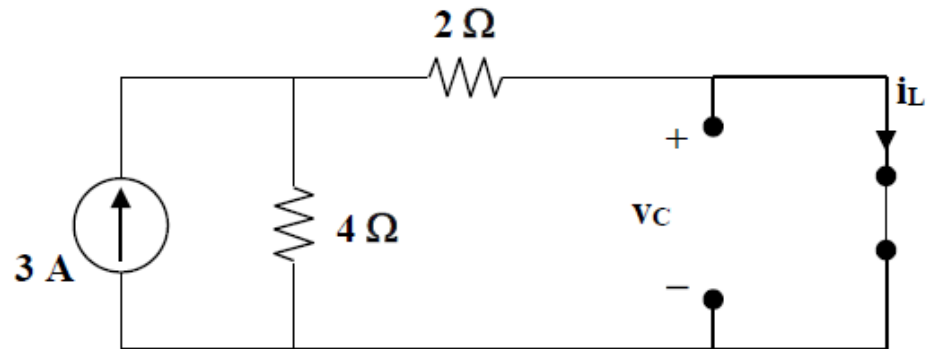Under dc conditions, the circuit is as shown below:



By current division,

$$i_L = \frac{4}{4+2}(3) = \mathbf{2A}, \quad v_C = \mathbf{0V}$$

$$w_L = \frac{1}{2}L i_L^2 = \frac{1}{2}\left(\frac{1}{2}\right)(2)^2 = \mathbf{1J}$$

$$w_C = \frac{1}{2}C v_C^2 = \frac{1}{2}(2)(0) = \mathbf{0J}$$

Solution 6.62

Consider the circuit in Fig. 6.84. Given that $v(t) = 12e^{-3t}$ mV for $t > 0$ and $i_1(0) = -30$ mA, find: (a) $i_2(0)$, (b) $i_1(t)$ and $i_2(t)$.

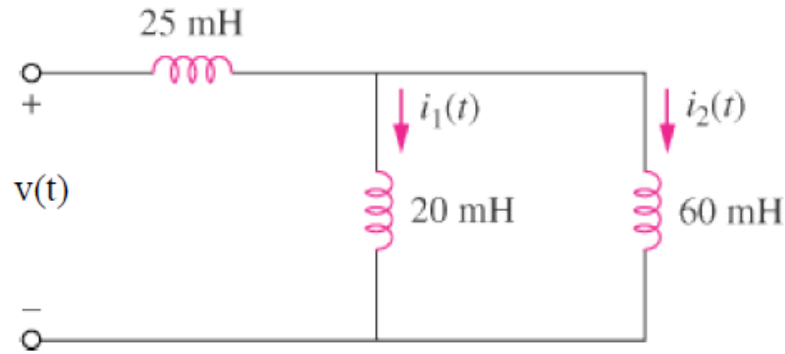


Figure 6.84
For Prob. 6.62.

Solution

$$(a) \quad L_{eq} = 25 + 20 \parallel 60 = 25 + \frac{20 \times 60}{80} = 40 \text{ mH}$$

$$v = L_{eq} \frac{di}{dt} \quad \longrightarrow \quad i = \frac{1}{L_{eq}} \int v(t) dt + i(0) = \frac{10^{-3}}{40 \times 10^{-3}} \int_0^t 12e^{-3t} dt + i(0) = -0.1(e^{-3t} - 1) + i(0)$$

Using current division and the fact that all the currents were zero when the circuit was put together, we get,

$$i_1 = \frac{60}{80} i = \frac{3}{4} i, \quad i_2 = \frac{1}{4} i$$

$$i_1(0) = \frac{3}{4} i(0) \quad \longrightarrow \quad 0.75i(0) = -0.03 \quad \longrightarrow \quad i(0) = -0.04$$

$$i_2 = \frac{1}{4} (-0.1e^{-3t} + 0.06) \text{ A} = (-25e^{-3t} + 15) \text{ mA}$$

$$i_2(0) = -25 + 15 = -10 \text{ mA.}$$


$$(b) \quad i_1(t) = 0.75(-0.1e^{-3t} + 0.06) = (-75e^{-3t} + 45) \text{ mA} \text{ and } i_2(t) = (-25e^{-3t} + 15) \text{ mA.}$$

Solution 6.73

Consider the op amp as shown below:

Let $v_a = v_b = v$
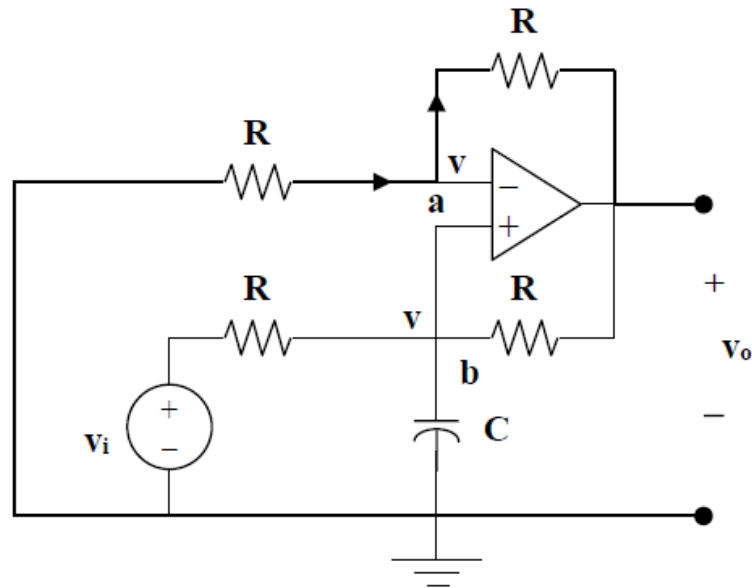
$$\text{At node a, } \frac{0 - v}{R} = \frac{v - v_o}{R} \longrightarrow 2v - v_o = 0 \quad (1)$$



$$\begin{aligned} \text{At node b, } \frac{v_i - v}{R} &= \frac{v - v_o}{R} + C \frac{dv}{dt} \\ v_i &= 2v - v_o + RC \frac{dv}{dt} \end{aligned} \quad (2)$$

Combining (1) and (2),

$$v_i = v_o - v_o + \frac{RC}{2} \frac{dv_o}{dt}$$

or

$$v_o = \frac{2}{RC} \int v_i dt$$

showing that the circuit is a noninverting integrator.